 



# Basic bistable element.

Figure 6.1




**SR latch. (a) Logic diagrams. (b) Function table where  $Q^+$  denotes the output  $Q$  in response to the inputs. (c) Two logic symbols.**

Figure 6.2

 


# An application of the *SR* latch. (a) Effects of contact bounce. (b) A switch debouncer.

Figure 6.3

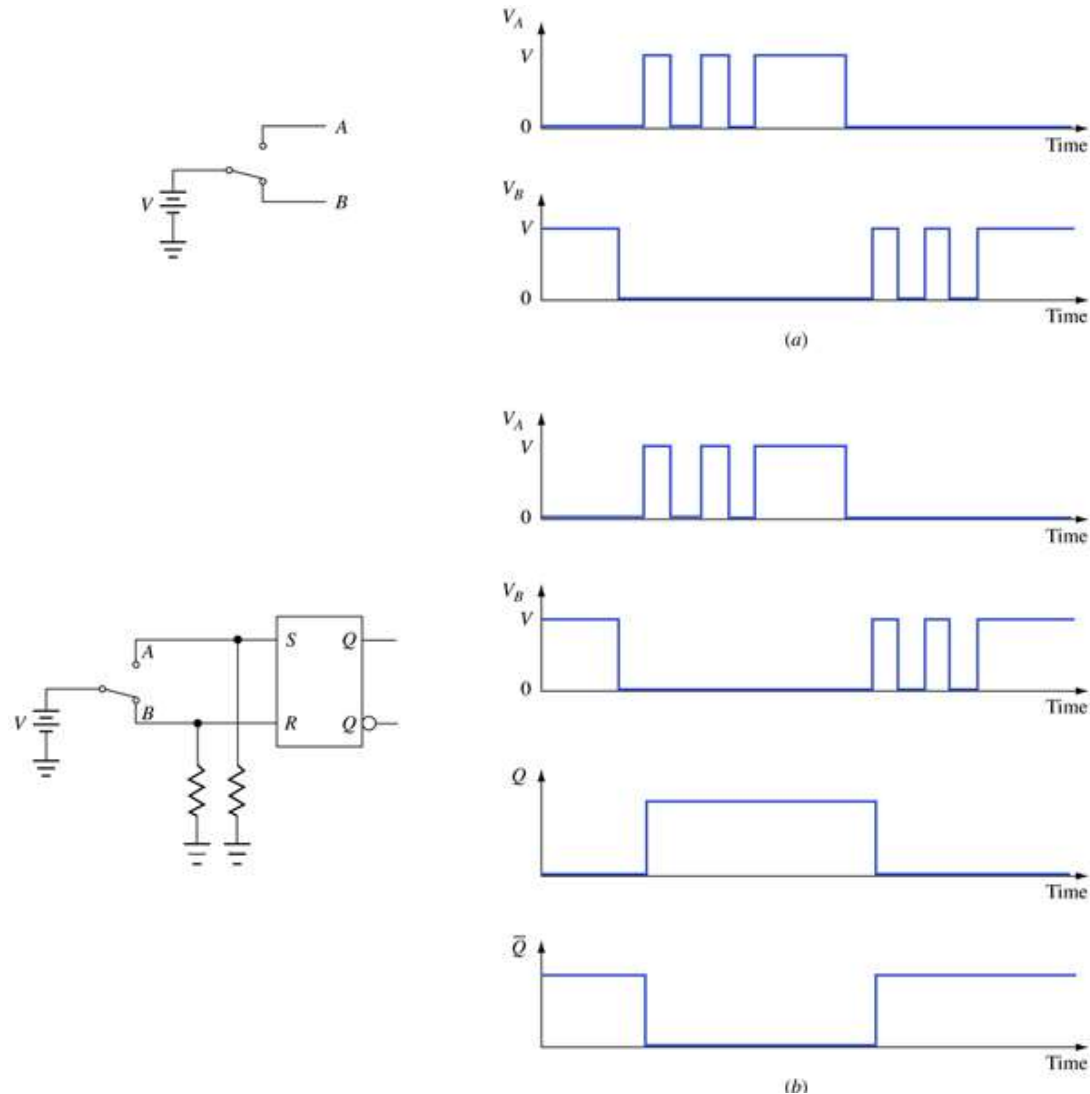


**$\overline{S}\overline{R}$ latch. (a) Logic diagrams. (b) Function table where  $Q^+$  denotes the output  $Q$  in response to the inputs. (c) Two logic symbols.**

Figure 6.4

 

**Gated  $SR$  latch. (a) Logic diagram. (b) Function table where  $Q^+$  denotes the output  $Q$  in response to the inputs. (c) Two logic symbols.**


Figure 6.5

 

Inputs			Outputs	
$S$	$R$	$C$	$Q^+$	$\bar{Q}^+$
0	0	1	$Q$	$\bar{Q}$
0	1	1	0	1
1	0	1	1	0
1	1	1	1*	1*
X	X	0	$Q$	$\bar{Q}$

\*Unpredictable behavior will result if  $S$  and  $R$  return to 0 simultaneously or  $C$  returns to 0 while  $S$  and  $R$  are 1


(b)

 

(c)


**Gated  $D$  latch. (a) Logic diagram. (b) Function table where  $Q^+$  denotes the output  $Q$  in response to the inputs. (c) Two logic symbols.**

Figure 6.6

 


Inputs		Outputs	
$D$	$C$	$Q^+$	$\bar{Q}^+$
0	1	0	1
1	1	1	0
X	0	$Q$	$\bar{Q}$

(b)

 


# Propagation delays in an *SR* latch.

Figure 6.7

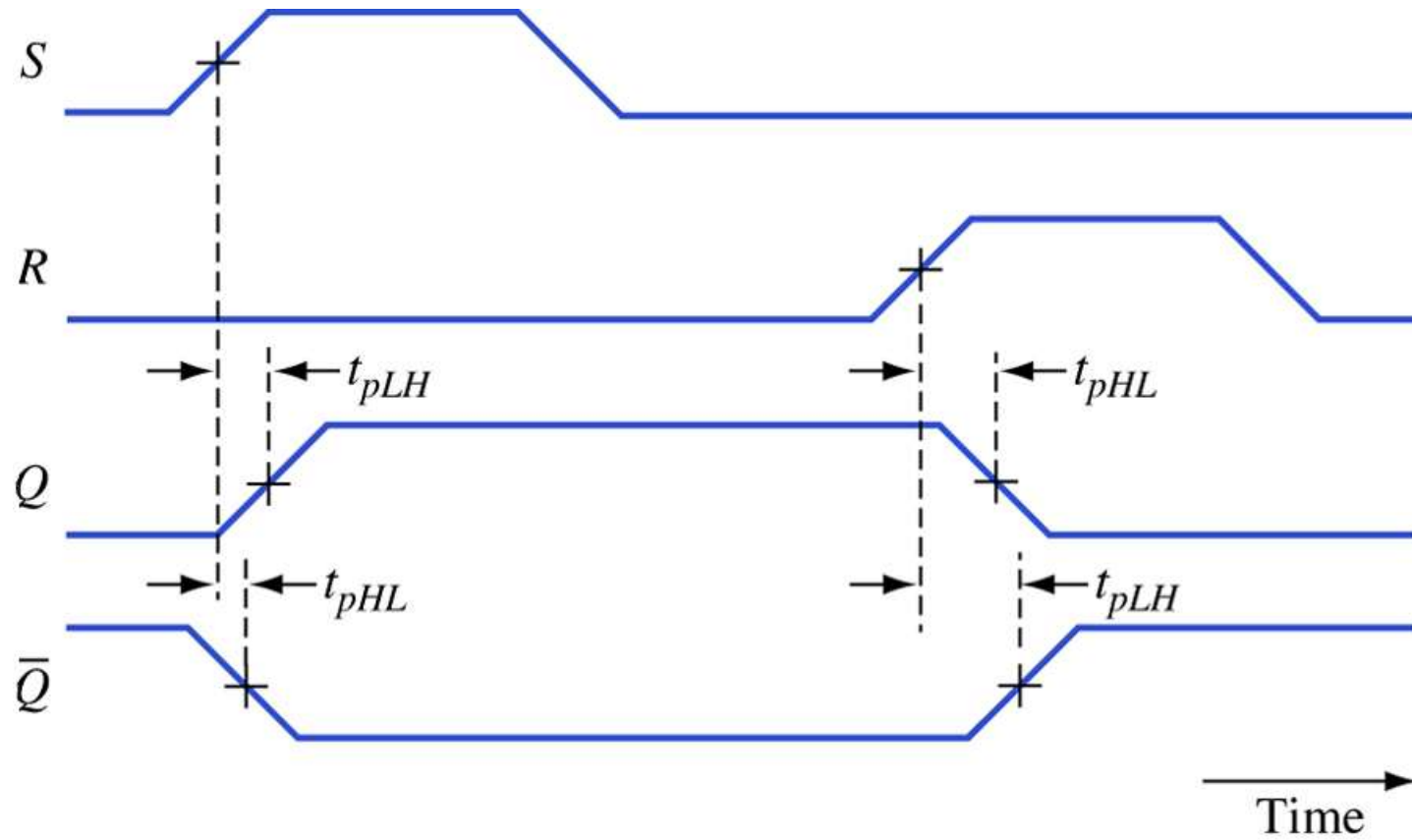

# Timing diagram for an *SR* latch.


Figure 6.8

 




# Minimum pulse width constraint.

Figure 6.9

 


# Timing diagram for a gated *D* latch.

Figure 6.10

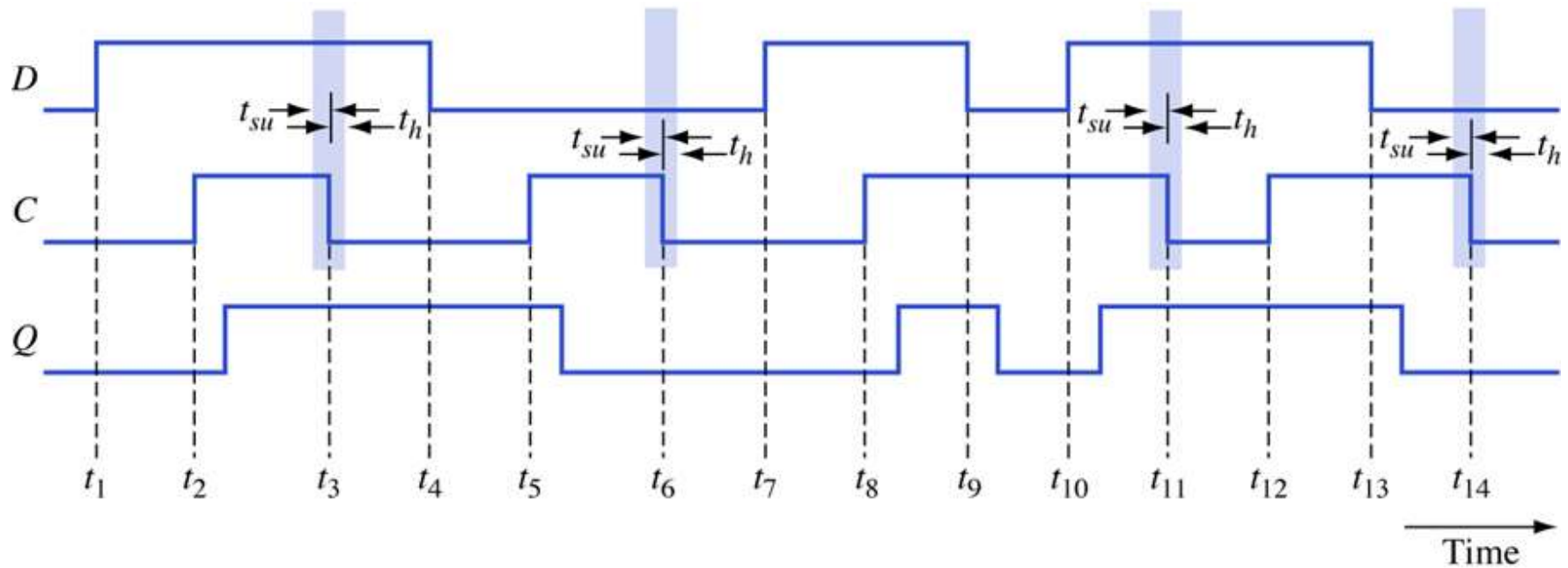


# Illustration of an unpredictable response in a gated *D* latch.

Figure 6.11

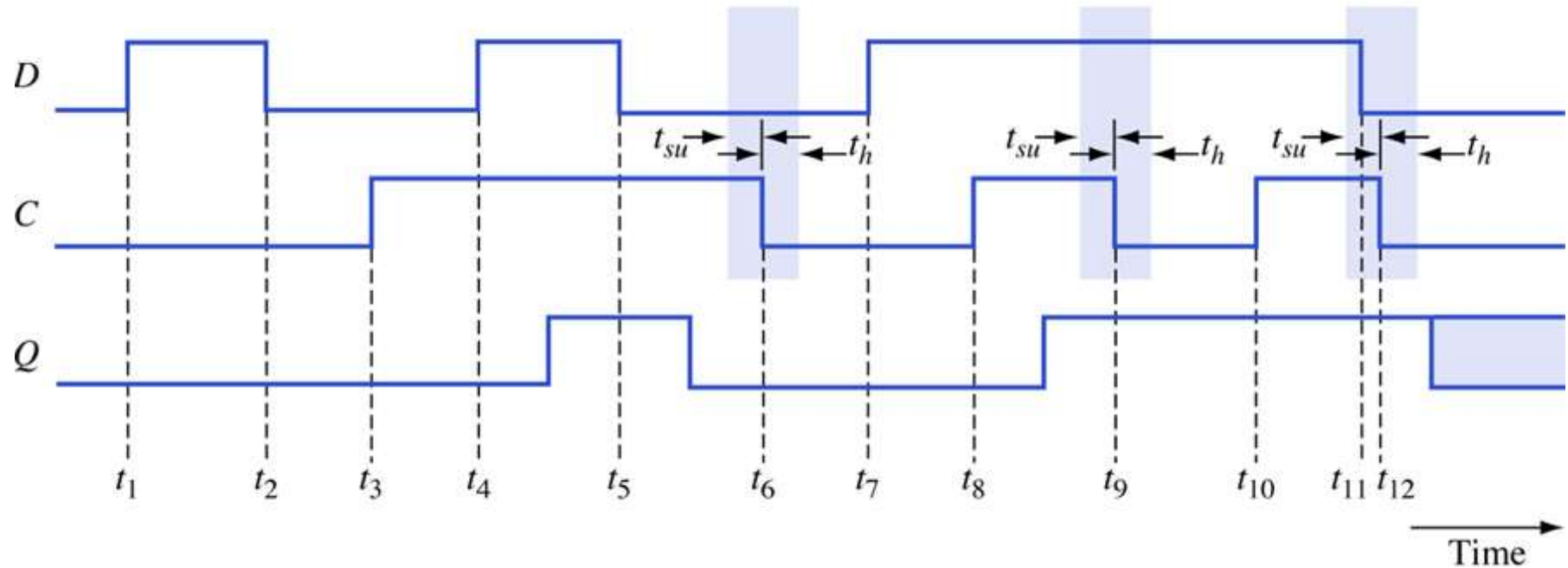


**Master-slave *SR* flip-flop. (a) Logic diagram using gated *SR* latches. (b) Flip-flop action during the control signal. (c) Function table where  $Q^+$  denotes the output  $Q$  in response to the inputs. (c) Two logic symbols.**

Figure 6.12

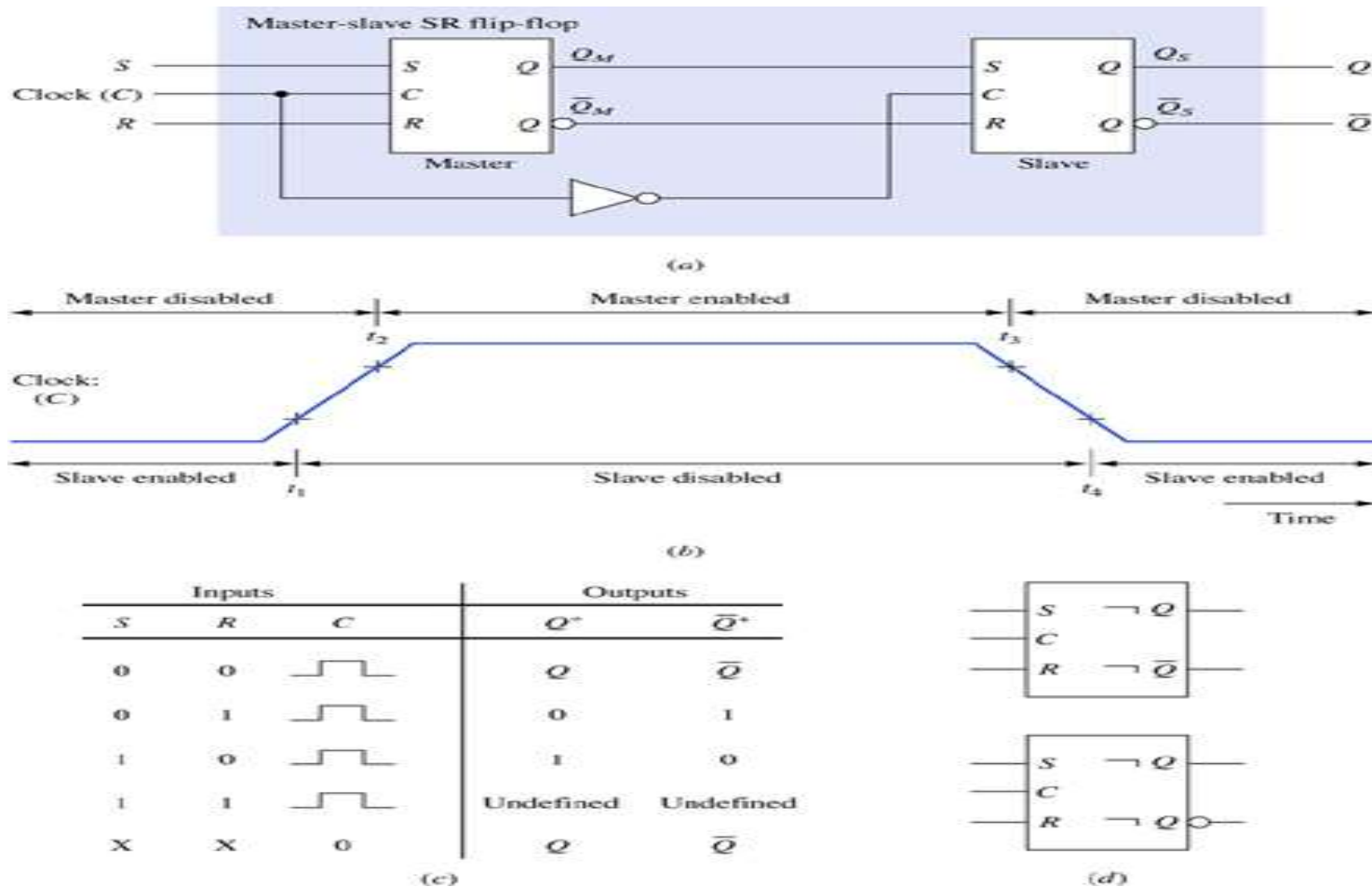


# Timing diagram for a master-slave *SR* flip-flop.



 

Figure 6.13

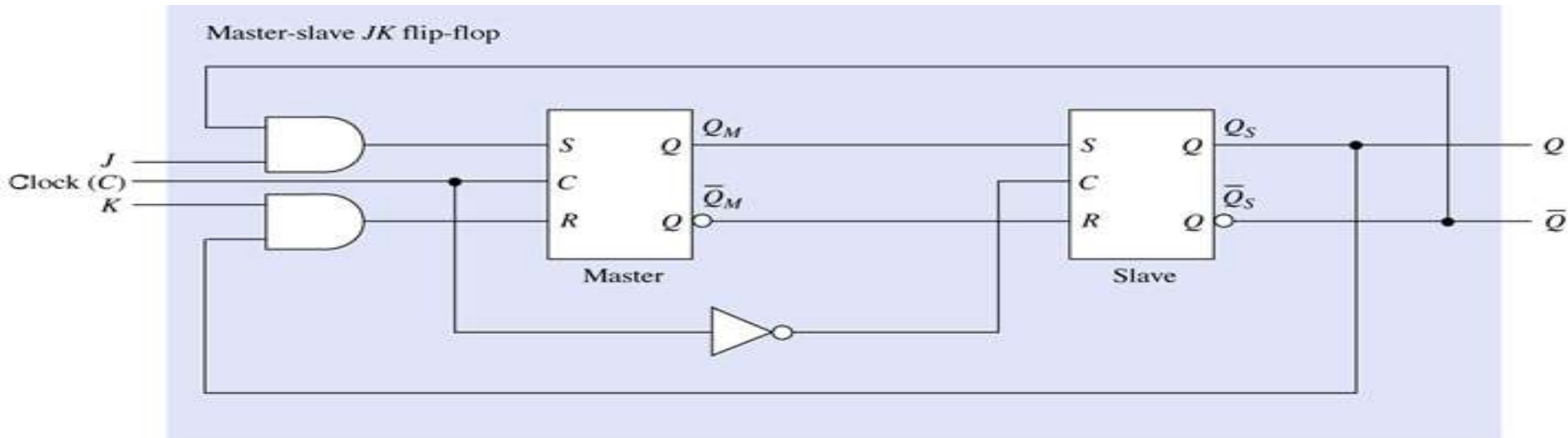



**Master-slave  $JK$  flip-flop. (a) Logic diagram using gated  $SR$  latches. (b) Function table where  $Q^+$  denotes the output  $Q$  in response to the inputs. (c) Two logic symbols.**



(a)

Inputs			Outputs	
$J$	$K$	$C$	$Q^+$	$\bar{Q}^+$
0	0		$Q$	$\bar{Q}$
0	1		0	1
1	0		1	0
1	1		$\bar{Q}$	$Q$
X	X	0	$Q$	$\bar{Q}$


(b)

  

(c)


# Timing diagram for master-slave *JK* flip-flop.

Figure 6.15

 


# Master-slave $D$ flip-flop. (a) Logic diagram using master-slave $SR$ flip-flop (b) Two logic symbols.

Figure 6.16

 

(a)

 


(b)




**Master-slave  $T$  flip-flop. (a) Logic diagram using a master-slave  $JK$  flip-flop. (b) Function table where  $Q^+$  denotes the output  $Q$  in response to the inputs. (c) Two logic symbols.**

F.

 

Inputs		Outputs	
$T$	$C$	$Q^+$	$\bar{Q}^+$
0		$Q$	$\bar{Q}$
1		$\bar{Q}$	$Q$
X	0	$Q$	$\bar{Q}$

 


(a)

(b)

(c)


**Positive-edge-triggered  $D$  flip-flop. (a) Logic diagram. (b) Function table where  $Q^+$  denotes the output  $Q$  in response to the inputs. (c) Two logic symbols.**

Figure

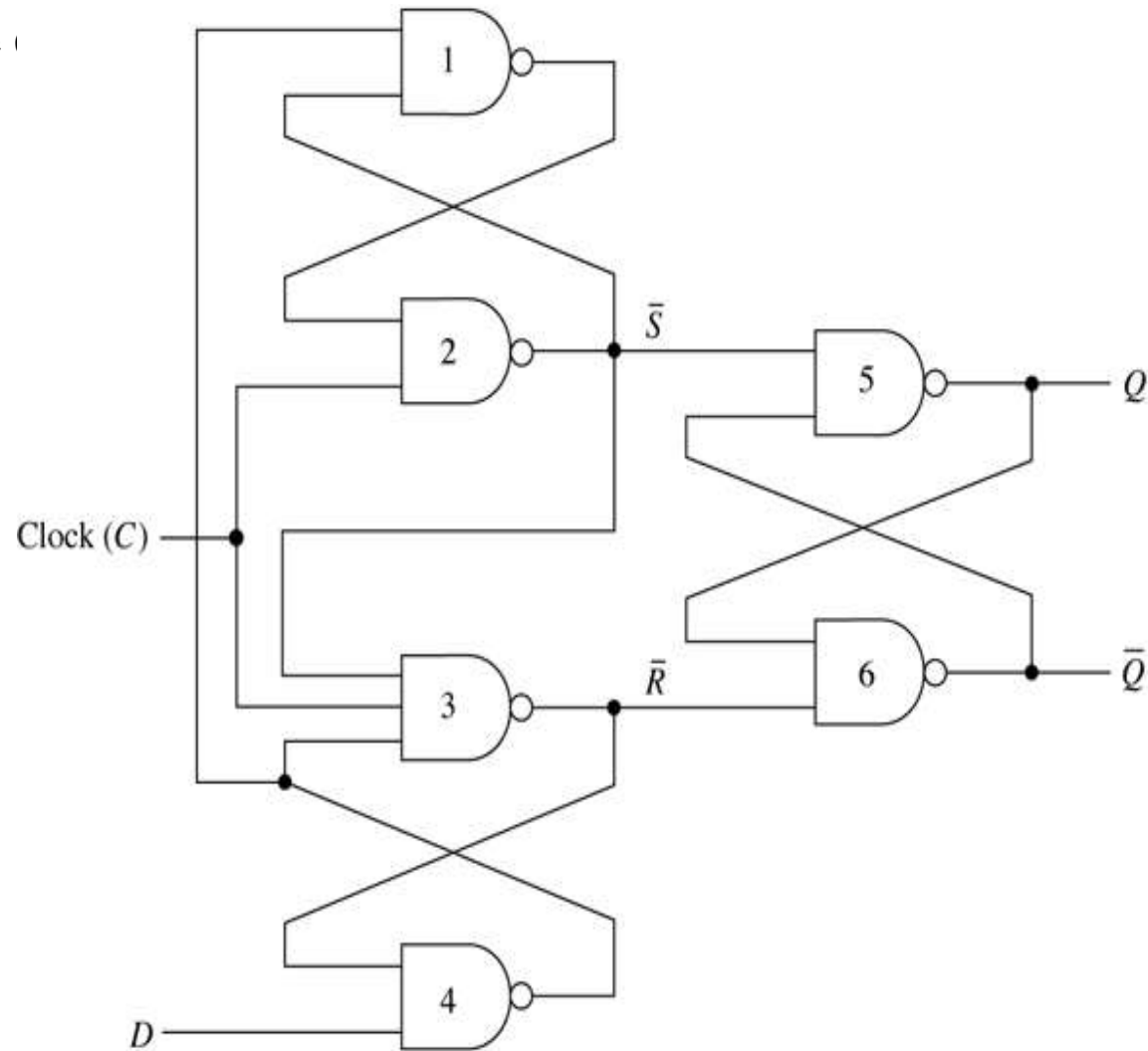

Inputs		Outputs	
$D$	$C$	$Q^+$	$\bar{Q}^+$
0	$\uparrow$	0	1
1	$\uparrow$	1	0
X	0	$Q$	$\bar{Q}$
X	1	$Q$	$\bar{Q}$


(b)

 

(c)

# Timing diagram for a positive-edge-triggered *D* flip-flop.

Figure 6.19


 


**Negative-edge-triggered  $D$  flip-flop. (a) Function table where  $Q^+$  denotes the output  $Q$  in response to the inputs. (b) Two logic symbols.**

Figure 6.20


Inputs		Outputs	
$D$	$Clk$	$Q^+$	$\bar{Q}^+$
0	↓	0	1
1	↓	1	0
X	0	$Q$	$\bar{Q}$
X	1	$Q$	$\bar{Q}$

(a)

  

(b)

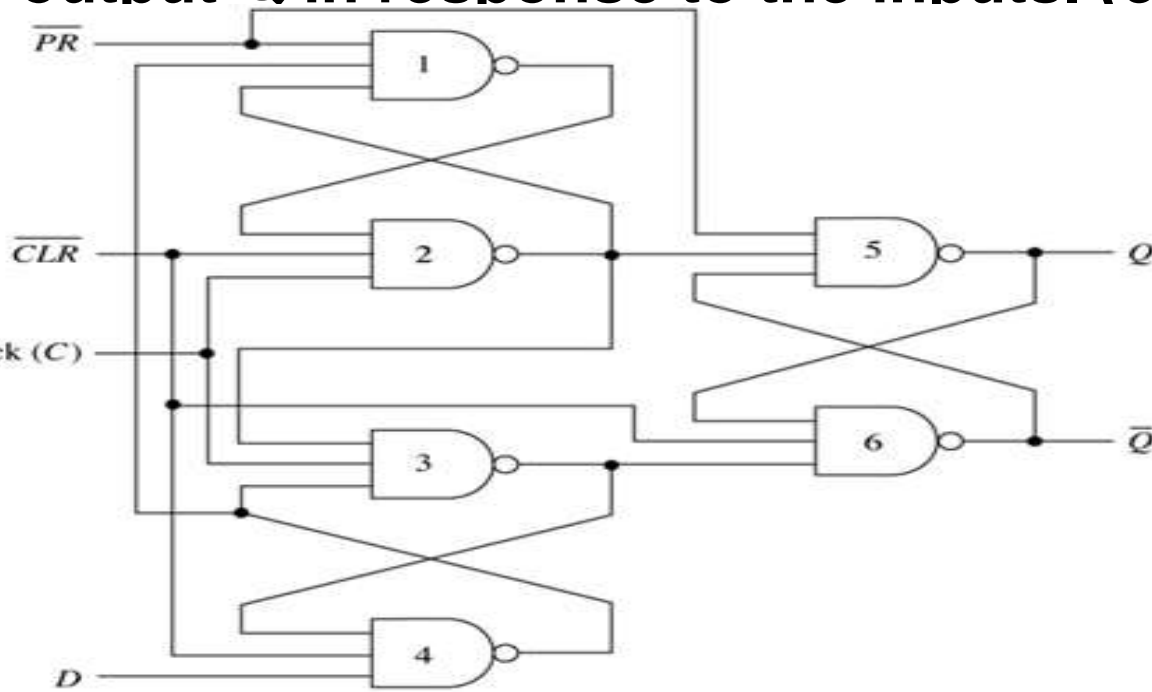**Positive-edge-triggered  $D$  flip-flop with asynchronous inputs.**  
**(a) Logic diagram. (b) Function table where  $Q^+$  denotes the output  $Q$  in response to the inputs. (c) Two logic symbols.**




(a)

Inputs				Outputs	
$\overline{PR}$	$\overline{CLR}$	$D$	$C$	$Q^+$	$\overline{Q}^+$
0	1	X	X	1	0
1	0	X	X	0	1
0	0	X	X	1*	1*
1	1	0	$\uparrow$	0	1
1	1	1	$\uparrow$	1	0
1	1	X	0	$Q$	$\overline{Q}$
1	1	X	1	$Q$	$\overline{Q}$

\*Unpredictable behavior will result if  $\overline{PR}$  and  $\overline{CLR}$  return to 1 simultaneously


(b)

 

(c)


**Positive-edge-triggered  $JK$  flip-flop. (a) Logic diagram. (b) Function table where  $Q^+$  denotes the output  $Q$  in response to the inputs. (c) Two logic symbols.**

Figure 6.22

 


Inputs			Outputs	
$J$	$K$	$C$	$Q^+$	$\bar{Q}^+$
0	0	$\uparrow$	$Q$	$\bar{Q}$
0	1	$\uparrow$	0	1
1	0	$\uparrow$	1	0
1	1	$\uparrow$	$\bar{Q}$	$Q$
X	X	0	$Q$	$\bar{Q}$
X	X	1	$Q$	$\bar{Q}$

(b)

 

**Positive-edge-triggered  $T$  flip-flop. (a) Logic diagram. (b) Function table where  $Q^+$  denotes the output  $Q$  in response to the inputs. (c) Two logic symbols.**


Figure 6.23

 

(a)

Inputs		Outputs	
$T$	$C$	$Q^+$	$\bar{Q}^+$
0	$\uparrow$	$Q$	$\bar{Q}$
1	$\uparrow$	$\bar{Q}$	$Q$
X	0	$Q$	$\bar{Q}$
X	1	$Q$	$\bar{Q}$


(b)

 


(c)

# Master-slave *JK* flip-flop with data lockout. (a) Logic diagram. (b) Two logic symbols.

Figure 6.24

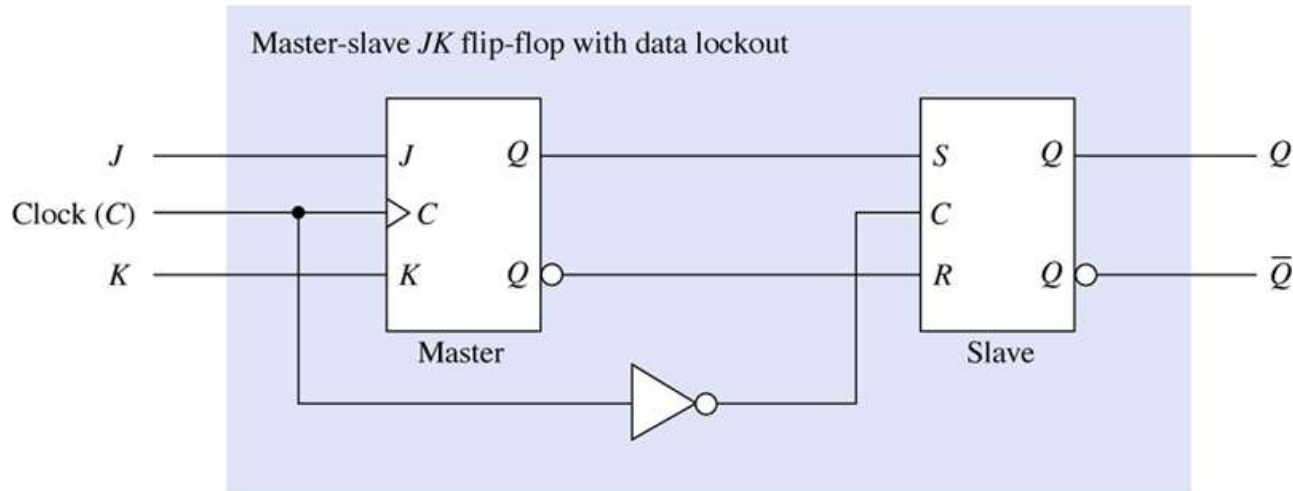

(a)

 

(b)



# Characteristic equations. (a) Derivation of characteristic equation for an *SR* flip-flop. (b) Summary of characteristic equations.

Figure 6.25

	<i>SR</i>			
	00	01	11	10
0	0	0	—	1
1	1	0	—	1

$$Q^+ = S + \bar{R}Q \quad (SR = 0)$$


(a)

Flip-flop type	Characteristic equation
<i>SR</i>	$Q^+ = S + \bar{R}Q \quad (SR = 0)$
<i>JK</i>	$Q^+ = J\bar{Q} + \bar{K}Q$
<i>D</i>	$Q^+ = D$
<i>T</i>	$Q^+ = T\bar{Q} + \bar{T}Q = T \oplus Q$

(b)


# Serial-in, serial-out unidirectional shift register.

Figure 6.26

 


# Serial-in, parallel-out unidirectional shift register.

Figure 6.27

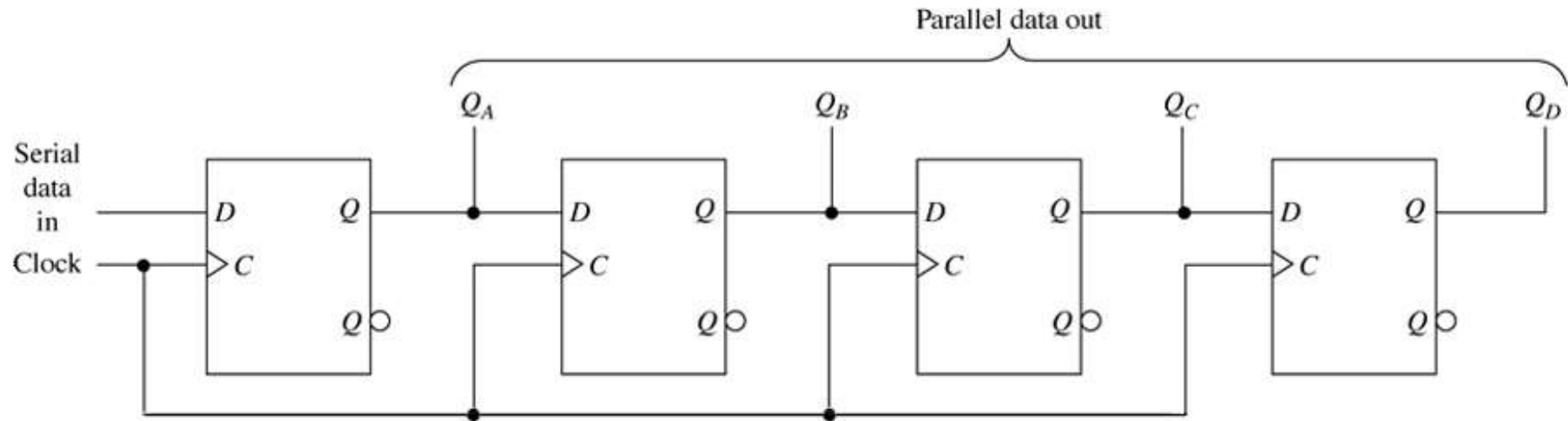



# Parallel-in unidirectional shift register.

Figure 6.28

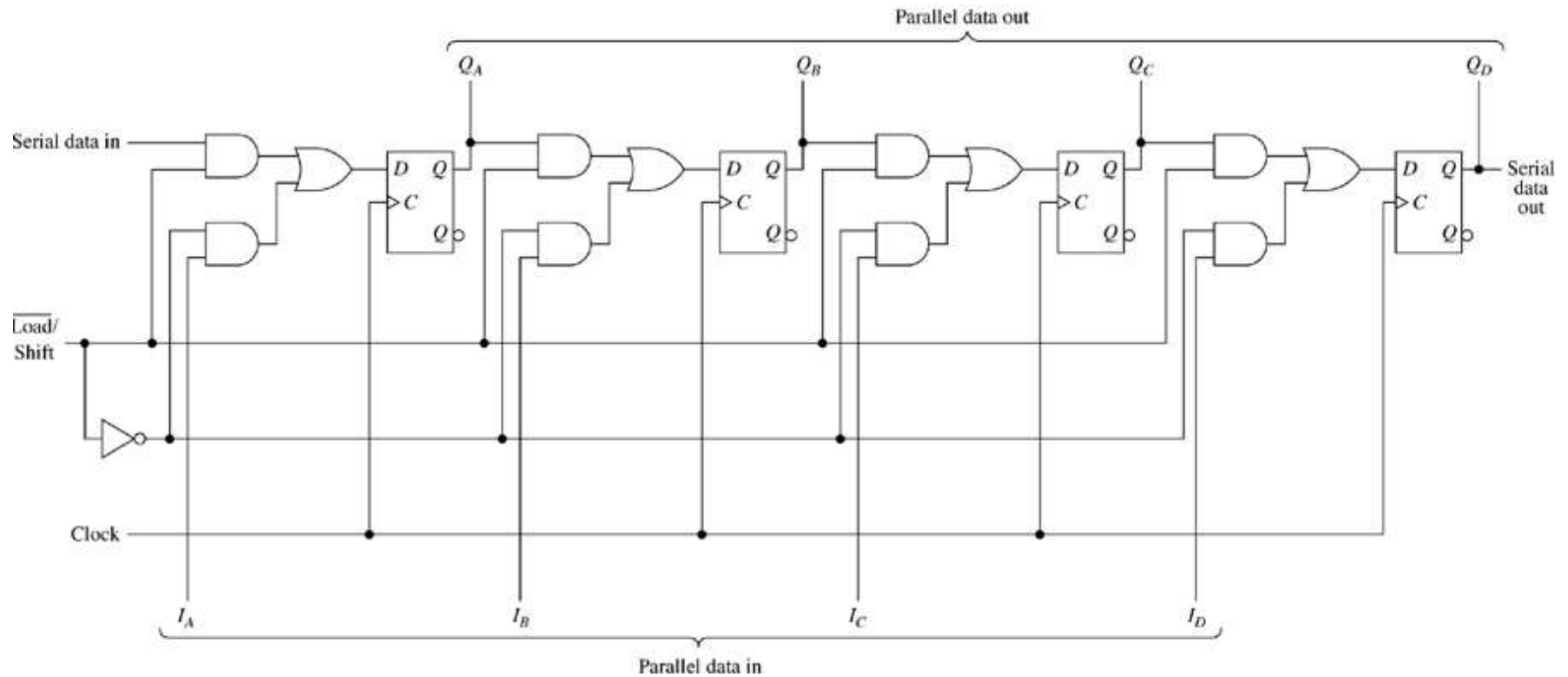

# Universal shift register. (a) Logic diagram. (b) Mode control. (c) Symbol.


Fig 1

 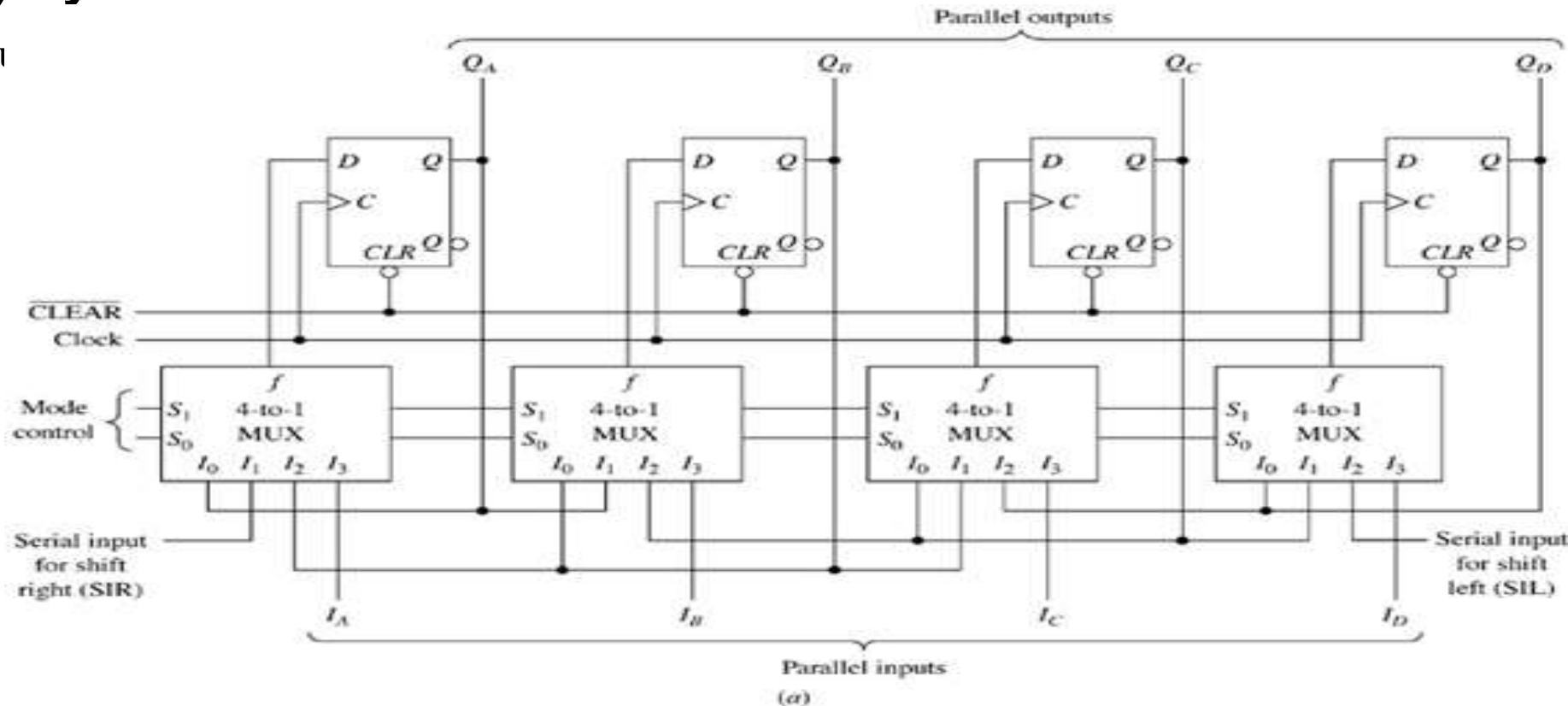


Select lines	Register operation
$S_1$ $S_0$	
0 0	Hold

# State diagram of a counter.

Figure 6.30

 

 
# Four-bit binary ripple counter. (a) Logic diagram. (b) Timing diagram. (c) Counting sequence.



(a)


$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1
0	0	0	0

(c)

 

# Four-bit synchronous binary counter.


Figure 6-32

 




# Four-bit synchronous binary counter variation.

Figure 6-22

 


# Four-bit synchronous binary counter with parallel load inputs. (a) Logic diagram. (b) Symbol.

Fig

 

# Synchronous mod-10 counter. (a) Connections. (b) Counting sequence.

Figure 6.35

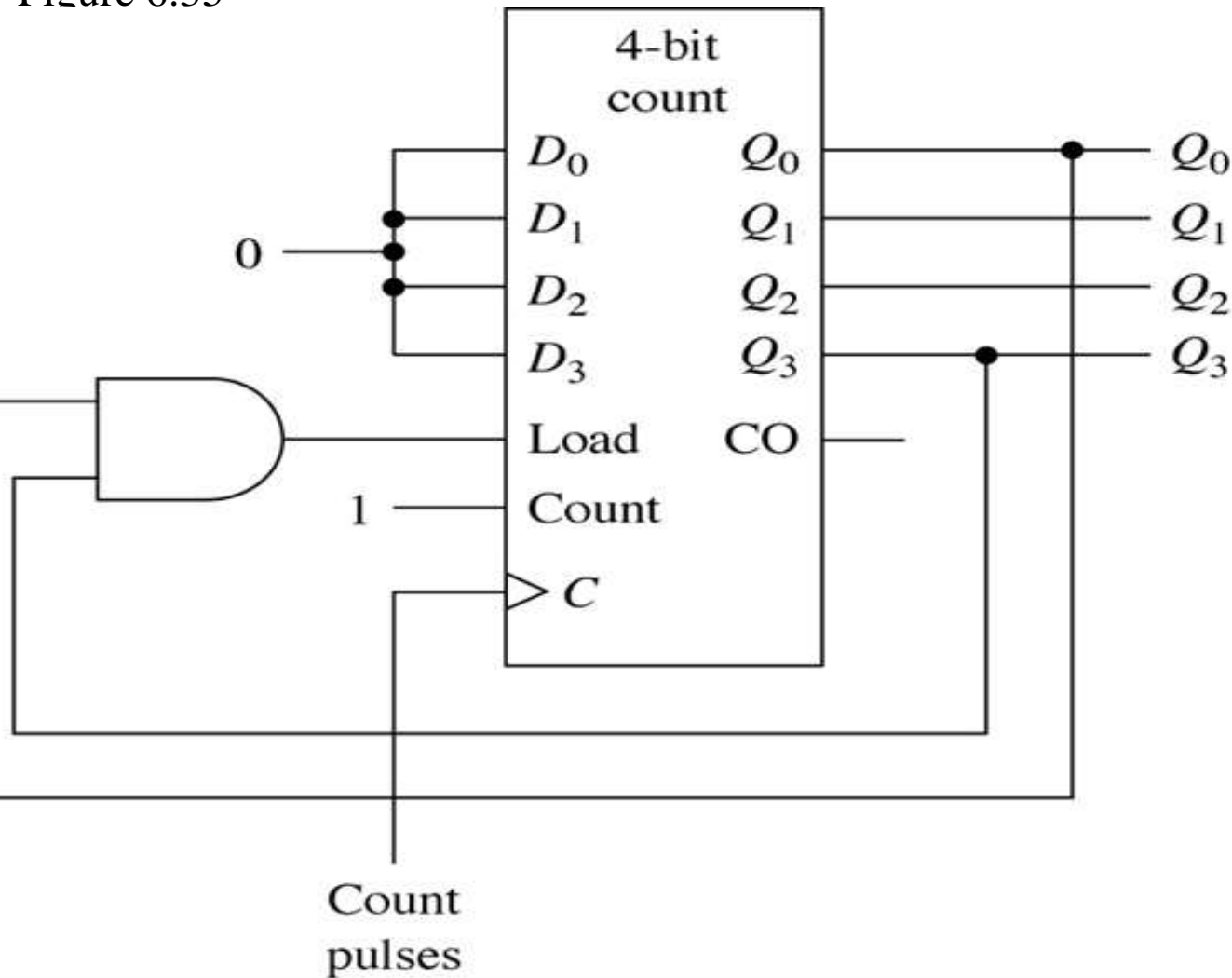


$Q_3$	$Q_2$	$Q_1$
0	0	0
0	0	0
0	0	1
0	0	1
0	1	0
0	1	0
0	1	1
0	1	1
1	0	0
1	0	0
<hr/>		
0	0	0
etc.		

(a)

(b)


# 8-bit synchronous binary counter constructed from two 4-bit synchronous binary counters.

Figure 6.36

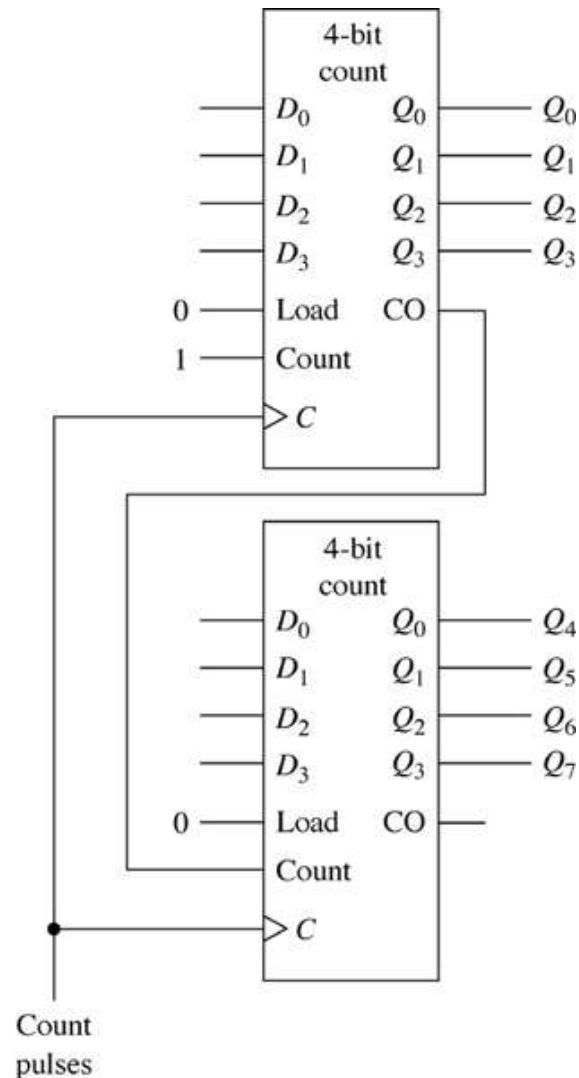

# Mod-4 ring counter. (a) Logic diagram. (b) Counting sequence.

Figure 6.37

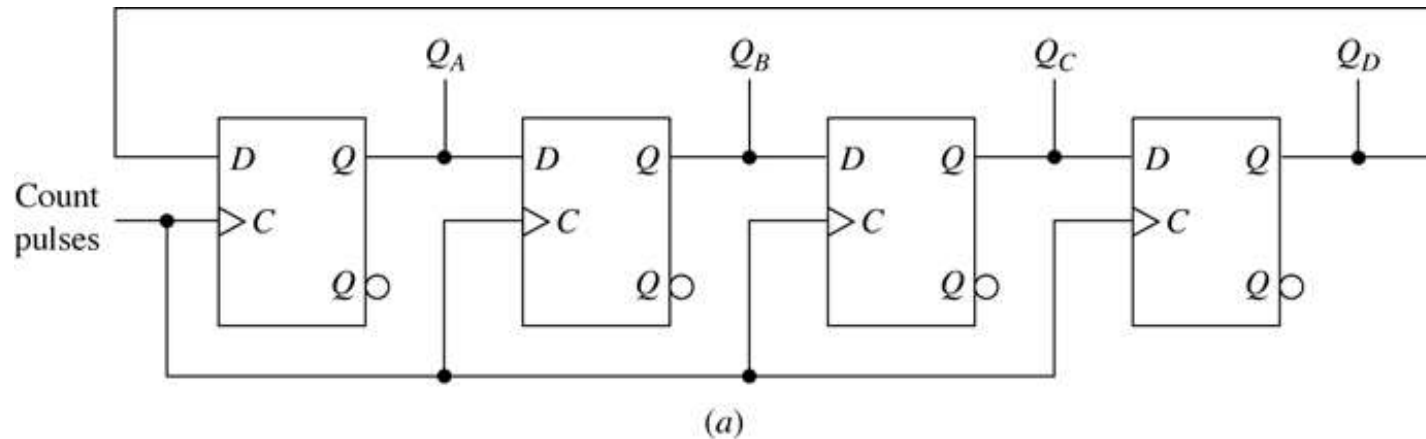


$Q_A$	$Q_B$	$Q_C$	$Q_D$
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1
<hr/>			
1	0	0	0
etc.			

(b)

# Mod-8 twisted-ring counter. (a) Logic diagram. (b) Counting sequence.

Figure 6.38

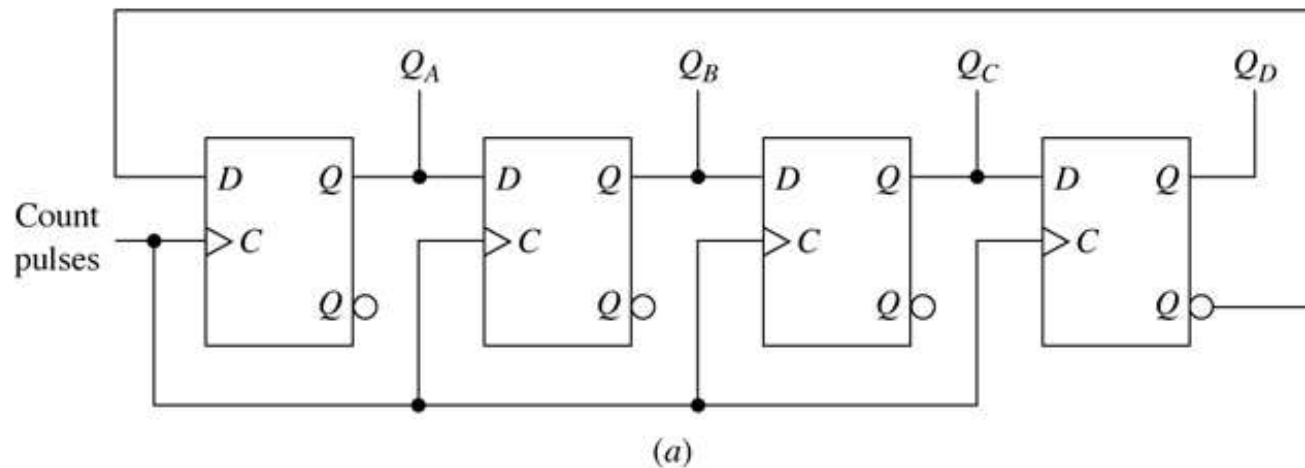


(b) Counting sequence.

$Q_A$	$Q_B$	$Q_C$	$Q_D$	And-gate inputs
0	0	0	0	$\overline{Q_A}\overline{Q_D}$
1	0	0	0	$Q_A\overline{Q_B}$
1	1	0	0	$Q_B\overline{Q_C}$
1	1	1	0	$Q_C\overline{Q_D}$
1	1	1	1	$Q_AQ_D$
0	1	1	1	$\overline{Q_A}Q_B$
0	0	1	1	$\overline{Q_B}Q_C$
0	0	0	1	$\overline{Q_C}Q_D$
0	0	0	0	etc.


# Mod-7 twisted-ring counter. (a) Logic diagram. (b) Counting sequence.

Figure 6.39

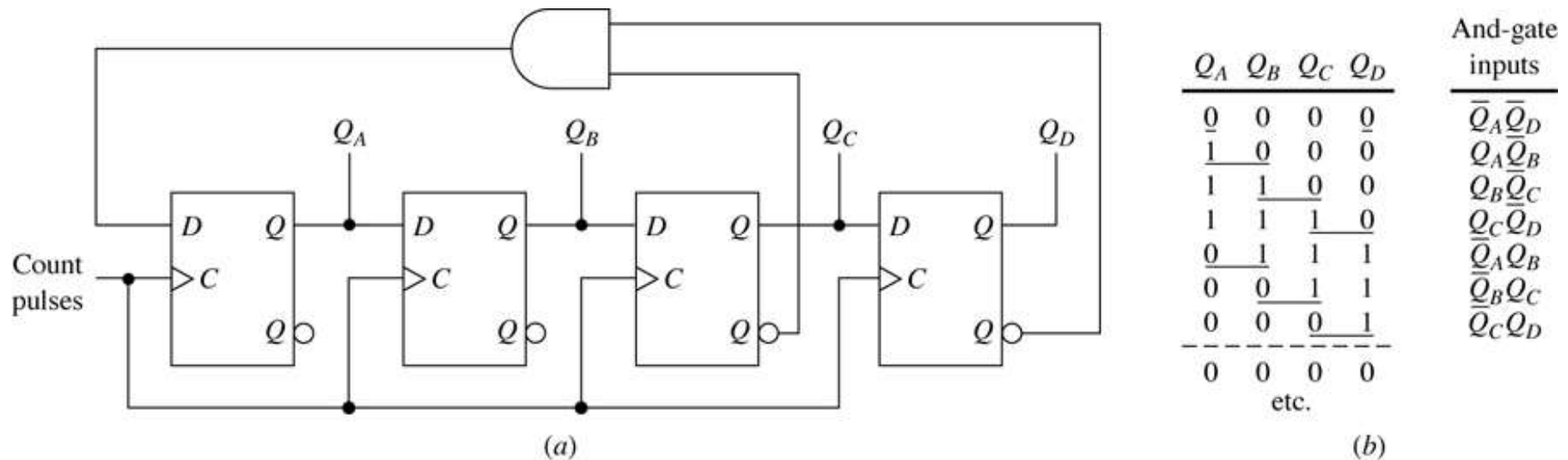

# General structure of a synchronous mod-6 counter using positive-edge-triggered *JK* flip-flops.


Figure 6.40

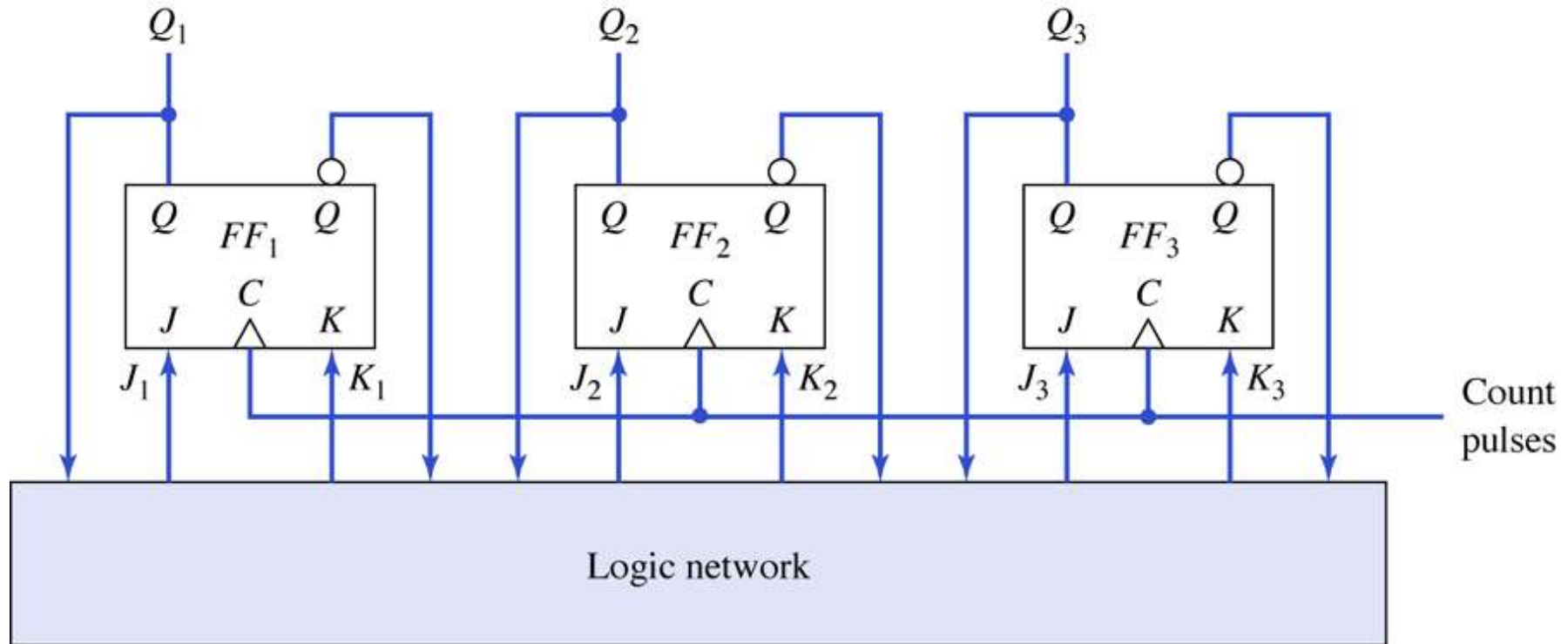




# Determination of the minimal-sum expressions for a synchronous mod-6 counter using clocked *JK* flip-flops.

Figure 6.41

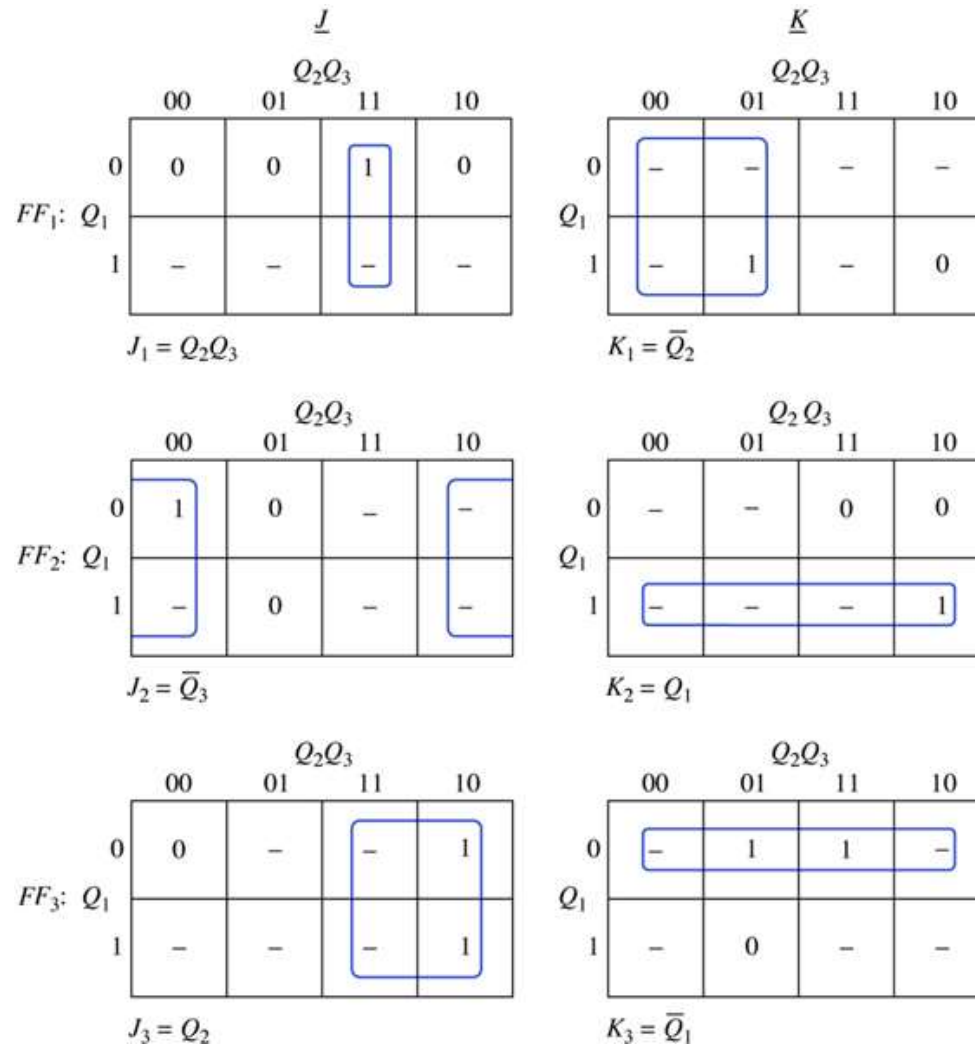




# Logic diagram of a synchronous mod-6 counter.

Figure 6.42

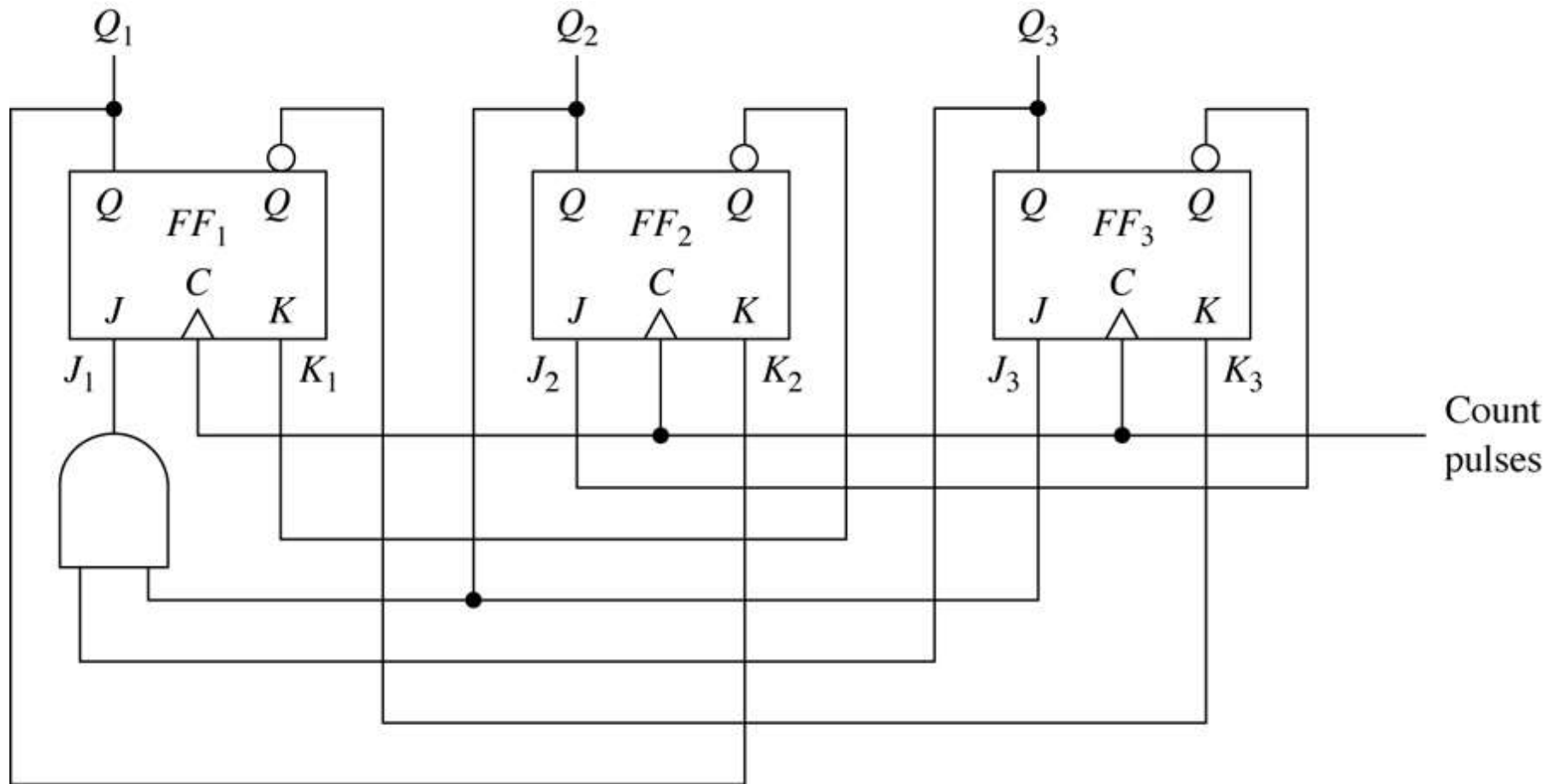

# Determination of the minimal-sum expressions for a synchronous mod-6 counter using clocked $D$ flip-flops.

Figure 6.43

   

# Determination of the minimal-sum expressions for a synchronous mod-6 counter using clocked $T$ flip-flops.

Figure 6.44

$T$

		$Q_2Q_3$			
		00	01	11	10
$FF_1: Q_1$	0	0	0	1	0
	1	-	1	-	0

$$T_1 = Q_1\bar{Q}_2 + Q_2Q_3$$

		$Q_2Q_3$			
		00	01	11	10
$FF_2: Q_1$	0	1	0	0	0
	1	-	0	-	1


$$T_2 = Q_1Q_2 + \bar{Q}_2\bar{Q}_3$$

		$Q_2Q_3$			
		00	01	11	10
$FF_3: Q_1$	0	0	1	1	1
	1	-	0	-	1

$$T_3 = Q_2 + \bar{Q}_1Q_3$$

# Determination of the minimal-sum expressions for a synchronous mod-6 counter using clocked SR flip-flops.

Figure 6.45

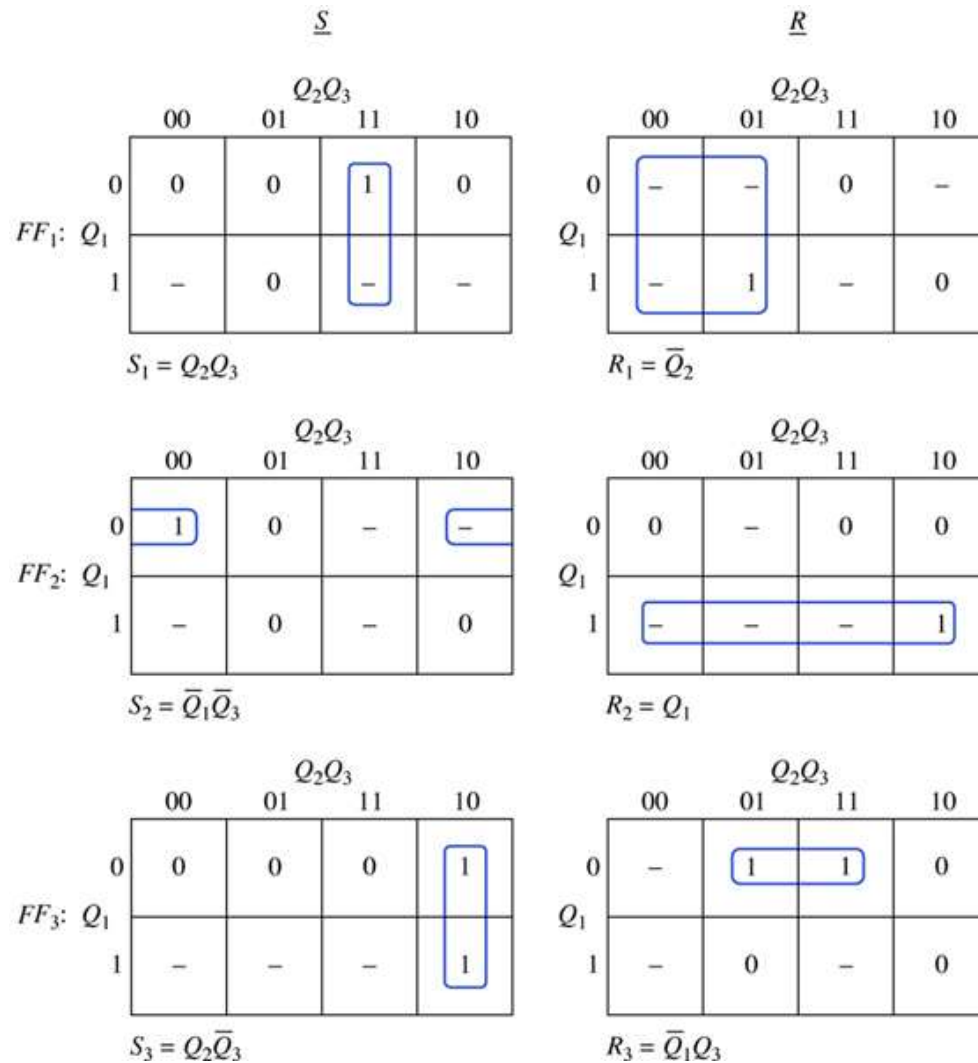

# Complete state diagram for the synchronous mod-6 counter of Fig. 6.42.

Figure 6.46

